



2/2022

King Abdulaziz University
Faculty of Engineering
Department of Electrical and Computer Engineering

EE 460: Digital Design II
Fibonacci Number Generator
Section: CA

Name	ID
Asaad Waleed Dadoush	1766585

Instructor
Dr. Mohammad Awedh

Contents

Introduction:	4
Top-level block diagram:	4
Fibonacci Number Generator:	5
Inside the block of Fibonacci Number Generator:	6
Datapath:	7
Control Unit:	8
Simulations and Testbench:	10

List of Figures

Figure 1: Top-level block diagram.....	4
Figure 2: Fibonacci Number Generator block.....	5
Figure 3: inside the block of Fibonacci Number Generator	6
Figure 4: Fibonacci Number Generator synthesis.....	7
Figure 5: Datapath diagram	7
Figure 6: Datapath synthesis.....	8
Figure 7: Control Unit block.....	8
Figure 8: Control Unit synthesis.....	9
Figure 9: State diagram.....	10
Figure 10: Testbench Results	10
Figure 11: Testbench code.....	10

Introduction:

This project is about designing a Fibonacci number generator that takes an input of n and outputs the Fibonacci number sum like $(n-1)$ and $(n-2)$ Fibonacci numbers, so the first two numbers in the sequence are 0 and 1, in the top-level module there are a control unit and a datapath, the control unit controls the data flow in the datapath, whenever the input is entered that can have a maximum value 24, the go signal will initial, then the control unit will take the n th number and start to send signals to the datapath to start to execute the operations, meanwhile, the counter will start counting until it reaches the specified value, the top-level design includes two outputs dataOut which is the results of the operation, and done signal, the done signal for receiving the results, this cycle can be repeated by including a reset signal.

Top-level block diagram:

This is the first step for the design starting with identifying all the required signals (inputs, outputs) then making sure all these signals that the design required.

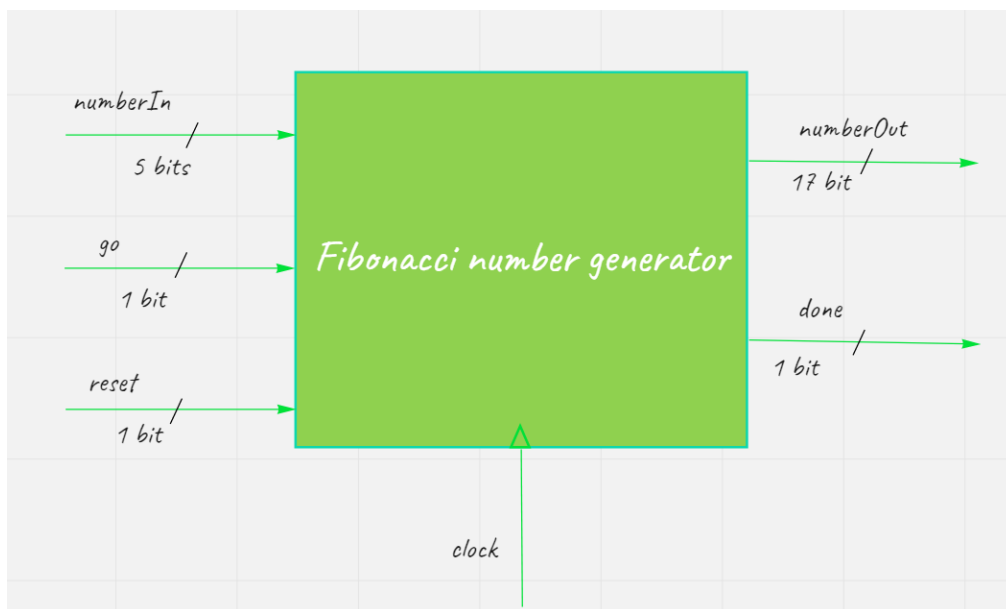


Figure 1: Top-level block diagram

Fibonacci Number Generator:

After making the top-level block now it is time to go deeper and identify the datapath and the control unit and all the signals and connections required for the design.

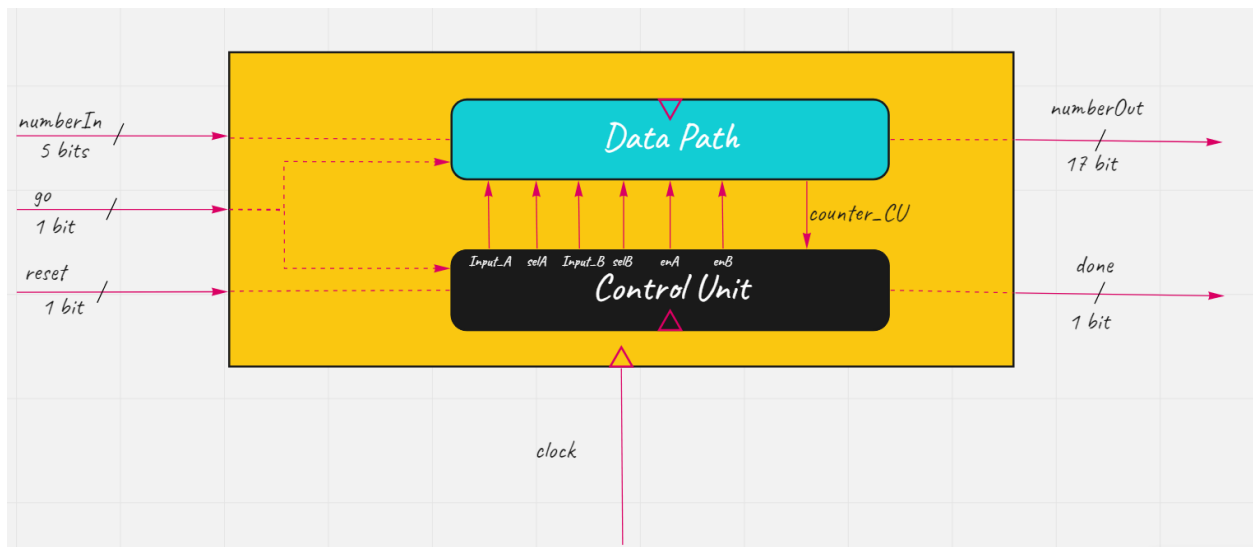


Figure 2: Fibonacci Number Generator block

Inside the block of Fibonacci Number Generator:

In this stage of design, it is time to start defining all the components that are needed for the design, so starting with defining inside each of the datapath and control units blocks as shown below.

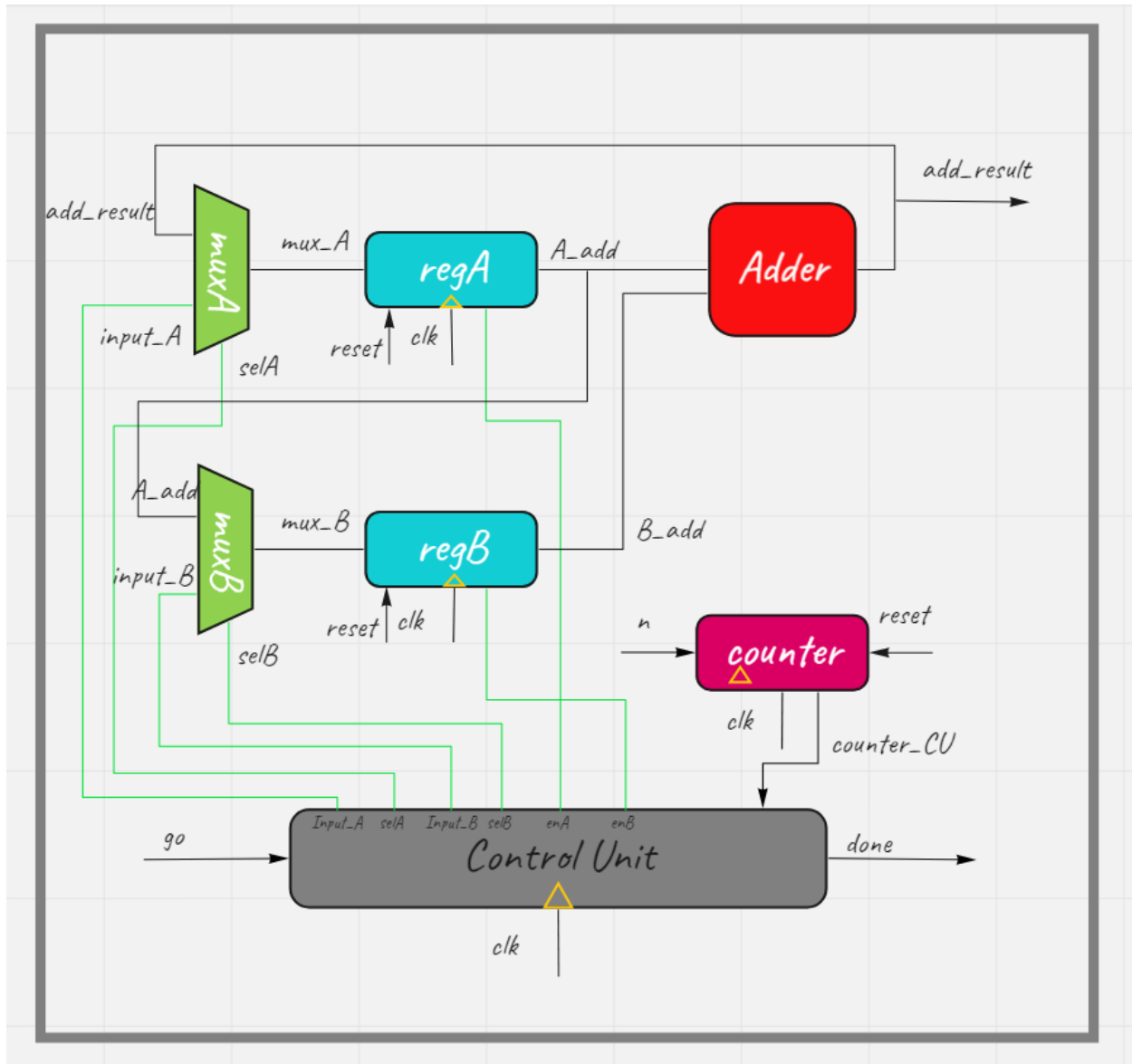


Figure 3: inside the block of Fibonacci Number Generator

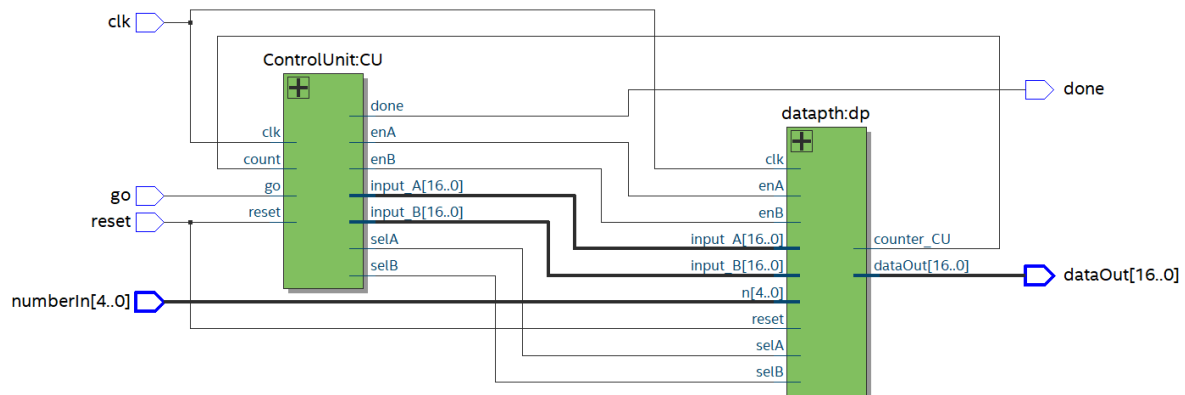


Figure 4: Fibonacci Number Generator synthesis

Datapath:

Let's have a deeper look inside the datapath and see what are the main computers inside it and how it works, how they get together to build the datapath.

 


Figure 5: Datapath diagram

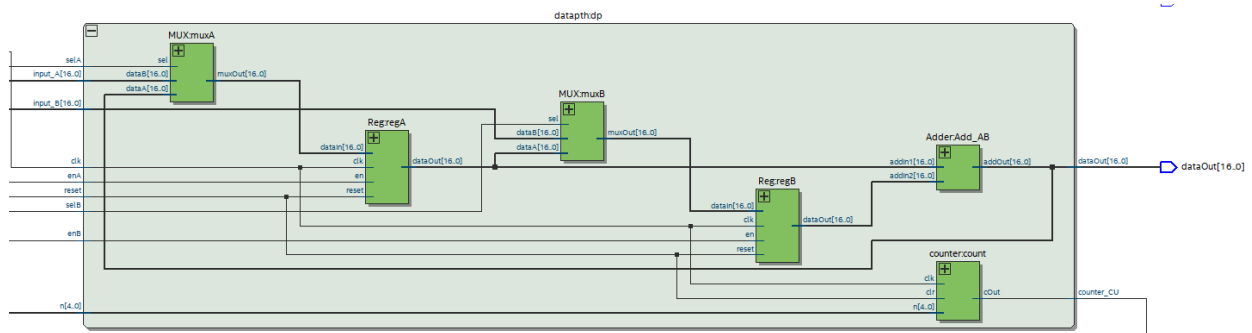


Figure 6: Datapath synthesis

As shown above in figure 5 the datapath block diagram and figure 6 inside the block diagram as shown inside the datapath the main components and the signals that come from the control unit to control the data flow in this datapath then the output which is the data out so for the main components there are 2 multiplexers for control the input for the two registers (regA, regB) then there is an adder for performing the addition operations, at last, the counter for the count the number of addition operations then send a signal to the control unit.

Control Unit:

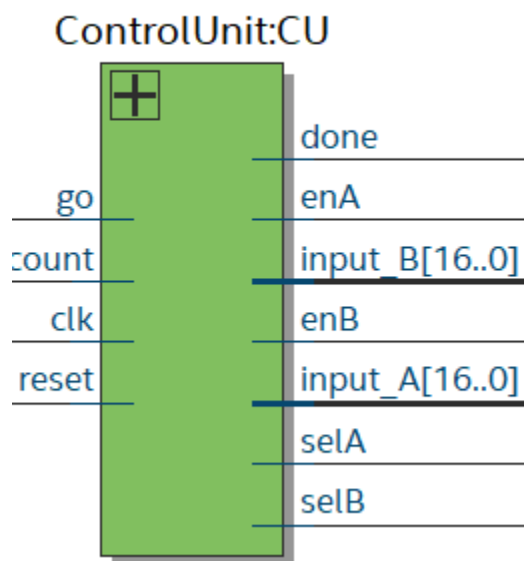


Figure 7: Control Unit block

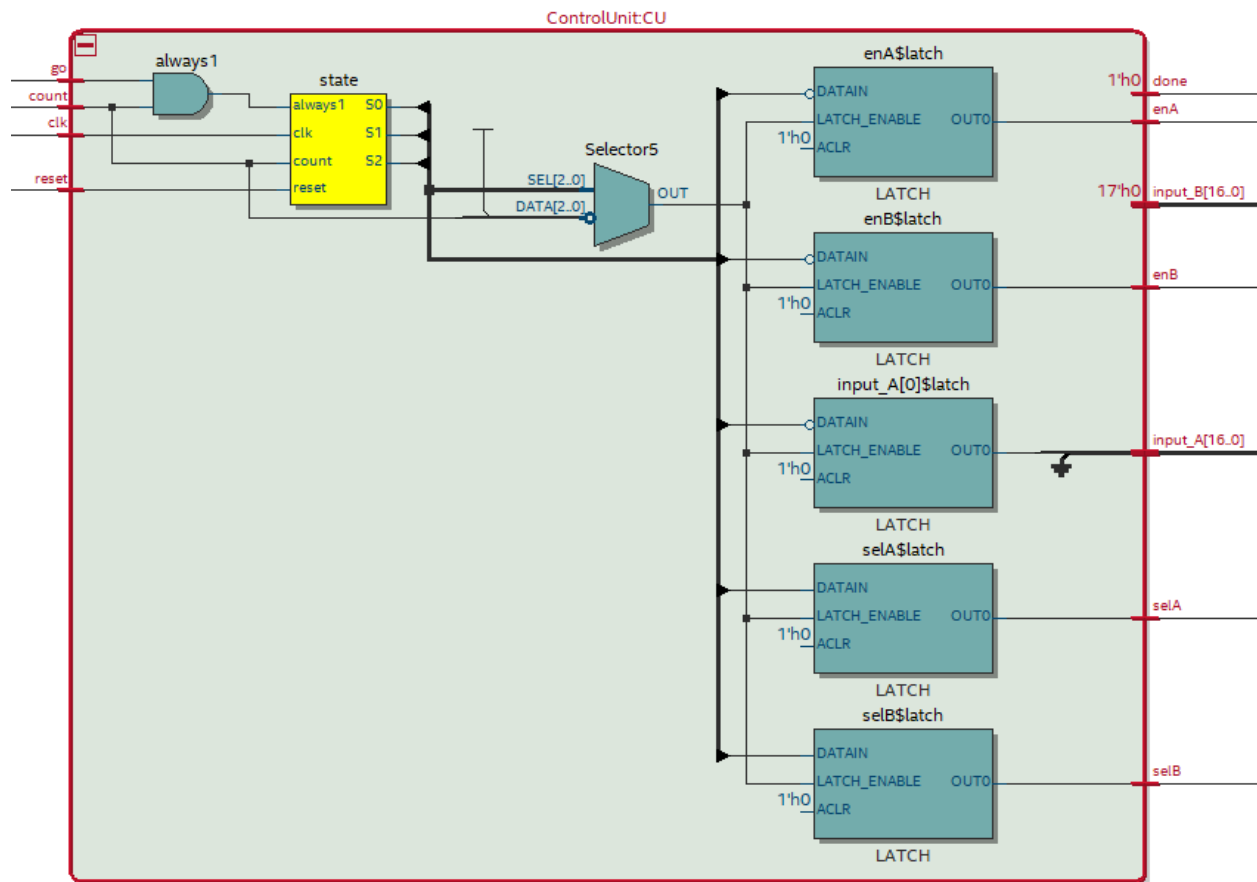


Figure 8: Control Unit synthesis

As shown in figure 8 the control unit has 4 inputs (go, count, CLK, reset) and 7 outputs so the inputs signals coming from the user go signal and form the datapath the count signal for the counter, in the control unit the output signals 5 of them to control the datapath and 2 of them for the first two inputs 1 and 0 (Input_A, Input_B).

 


Figure 9: State diagram

Simulations and Testbench:

 


Figure 10: Testbench Results

```

always
  #5 clk = ~clk;

initial begin
  // initial the values
  n = 0;
  go = 0;
  reset = 1; // the reset signal to remove the redline in the first number of the outputs in the wave
  clk = 0;
  #1 // just give a small pulse for the reset signal
  reset = 0;

  @(posedge clk);
  n = 24; // max 24
  go = 0;

  @(posedge clk);
  n = 24;
  go = 1; // start counting
  #400;
  $stop;
  
```

Figure 11: Testbench code